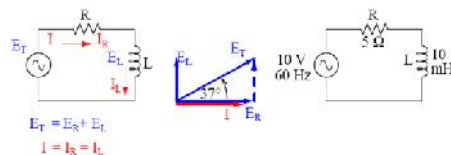


MEE210 Electrical Machines

L03 AC Circuit Analysis & Power Calculations

L02 Alternating Voltage and Current

AC circuit –RL in series



Inductive reactance of the coil

$$X_L = 0 + 3.7699j\Omega$$

The total effect is called as **impedance**.

$$Z = R + X_L = 5 + 3.7699j\Omega = 6.262\angle 37.016^\circ\Omega$$

$$Z = \frac{V}{I}$$

$$I = \frac{10\angle 0^\circ V}{6.262\angle 37.016^\circ\Omega} = 1.597\angle -37.016^\circ A$$

Dr. Levent ÇETİN

L02 Alternating Voltage and Current

AC circuit –RL in series

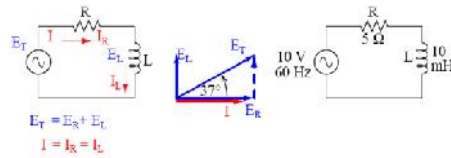
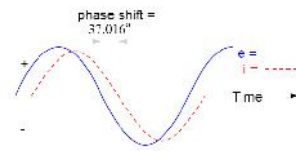
Figure 3.10: Series resistor inductor circuit: Current lags applied voltage by 0° to 90° .

Figure 3.11: Current lags voltage in a series L-R circuit.

$$E = IZ$$

$$E = IZ$$

$$E_R = I_R Z_R$$

$$E_L = I_L Z_L$$

$$E_R = (1.597 \text{ A} \angle -37.016^\circ)(5 \Omega \angle 0^\circ)$$

$$E_L = (1.597 \text{ A} \angle -37.016^\circ)(3.7699 \Omega \angle 90^\circ)$$

$$E_R = 7.9847 \text{ V} \angle -37.016^\circ$$

$$E_L = 6.0203 \text{ V} \angle 52.984^\circ$$

Notice that the phase angle of E_L is exactly 90° more than the phase angle of the current.

$$E_{\text{total}} = E_R + E_L$$

$$E_{\text{total}} = (7.9847 \text{ V} \angle -37.016^\circ) + (6.0203 \text{ V} \angle 52.984^\circ)$$

$$E_{\text{total}} = 10 \text{ V} \angle 0^\circ$$

Dr. Levent ÇETİN

L02 Alternating Voltage and Current

AC circuit –RL in parallel

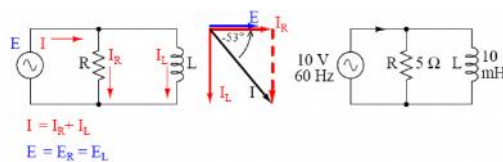


Figure 3.14: Parallel R-L circuit.

	R	L	Total	
E	10 + j0 10 \angle 0°	10 + j0 10 \angle 0°	10 + j0 10 \angle 0°	Volts
I				Amps
Z	5 + j0 5 \angle 0°	0 + j3.7699 3.7699 \angle 90°		Ohms

Rule of parallel circuits:

$$E_{\text{total}} = E_R = E_L$$

Dr. Levent ÇETİN

L02 Alternating Voltage and Current

AC circuit –RL in parallel

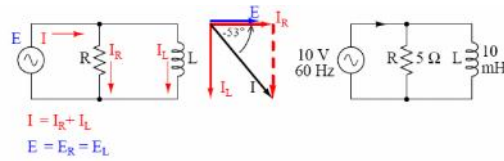


Figure 3.14: Parallel R-L circuit.

	R	L	Total	
E	10 + j0 10 ∠ 0°	10 + j0 10 ∠ 0°	10 + j0 10 ∠ 0°	Volts
I	2 + j0 2 ∠ 0°	0 - j2.6526 2.6526 ∠ -90°		Amps
Z	5 + j0 5 ∠ 0°	0 + j3.7699 3.7699 ∠ 90°		Ohms

\uparrow Ohm's Law $I = \frac{E}{Z}$ \uparrow Ohm's Law $I = \frac{E}{Z}$

Dr. Levent ÇETİN

L02 Alternating Voltage and Current

AC circuit –RL in parallel

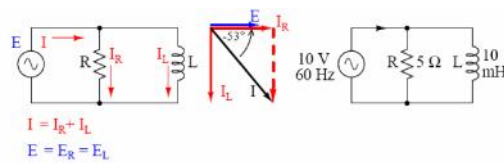


Figure 3.14: Parallel R-L circuit.

	R	L	Total	
E	10 + j0 10 ∠ 0°	10 + j0 10 ∠ 0°	10 + j0 10 ∠ 0°	Volts
I	2 + j0 2 ∠ 0°	0 - j2.6526 2.6526 ∠ -90°	2 - j2.6526 3.3221 ∠ -52.984°	Amps
Z	5 + j0 5 ∠ 0°	0 + j3.7699 3.7699 ∠ 90°		Ohms

Rule of parallel circuits:

$$I_{\text{total}} = I_R + I_L$$

Dr. Levent ÇETİN

L02 Alternating Voltage and Current

AC circuit –RL in parallel

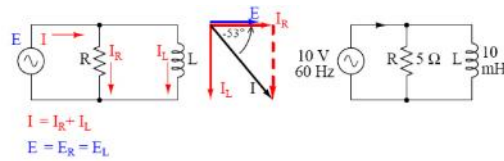


Figure 3.14: Parallel R-L circuit.

	R	L	Total	
E	$10 + j0$ $10 \angle 0^\circ$	$10 + j0$ $10 \angle 0^\circ$	$10 + j0$ $10 \angle 0^\circ$	Volts
I	$2 + j0$ $2 \angle 0^\circ$	$0 - j2.6526$ $2.6526 \angle -90^\circ$	$2 - j2.6526$ $3.322 \angle -52.984^\circ$	Amps
Z	$5 + j0$ $5 \angle 0^\circ$	$0 + j3.7699$ $3.7699 \angle 90^\circ$	$1.8122 + j2.4035$ $3.0102 \angle 52.984^\circ$	Ohms

Ohm's Law
 $Z = \frac{E}{I}$

or


Rule of parallel circuits:

$$Z_{\text{total}} = \frac{1}{\frac{1}{Z_R} + \frac{1}{Z_L}}$$

Dr. Levent ÇETİN

L02 Alternating Voltage and Current

AC circuit –RC in series

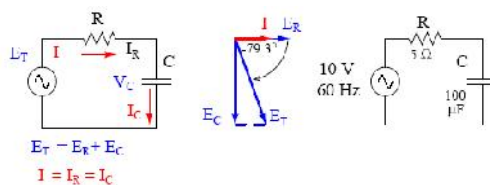

$$X_C = 0 - 26.5258j \Omega$$

$$R = 5 + 0j \Omega$$

$$Z = R + X_C = 5 - 26.5258j \Omega = 26.993 \angle -79.325^\circ$$

$$I = \frac{E}{Z}$$

$$I = \frac{10 \text{ V} \angle 0^\circ}{26.933 \Omega \angle -79.325^\circ}$$

$$I = 370.5 \text{ mA} \angle 79.325^\circ$$


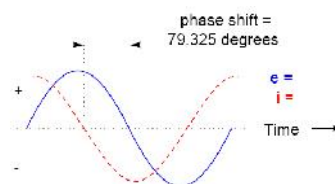


Figure 4.11: Voltage lags current (current leads voltage) in a series R-C circuit.

Dr. Levent ÇETİN

L02 Alternating Voltage and Current

AC circuit –RC in series

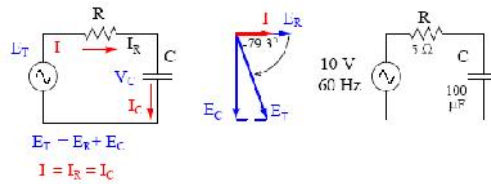

	R	C	Total	
E			$10 + j0$ $10 \angle 0^\circ$	Volts
I			$68.623m + j364.06m$ $370.5m \angle 79.325^\circ$	Amps
Z	$5 + j0$ $5 \angle 0^\circ$	$0 - j26.5258$ $26.5258 \angle -90^\circ$	$5 - j26.5258$ $26.993 \angle -79.325^\circ$	Ohms


	R	C	Total	
E			$10 + j0$ $10 \angle 0^\circ$	Volts
I	$68.623m + j364.06m$ $370.5m \angle 79.325^\circ$	$68.623m + j364.06m$ $370.5m \angle 79.325^\circ$	$68.623m + j364.06m$ $370.5m \angle 79.325^\circ$	Amps
Z	$5 + j0$ $5 \angle 0^\circ$	$0 - j26.5258$ $26.5258 \angle -90^\circ$	$5 - j26.5258$ $26.993 \angle -79.325^\circ$	Ohms

Rule of series circuits:
 $I_{total} = I_R = I_C$

Dr. Levent ÇETİN

L02 Alternating Voltage and Current

AC circuit –RC in series

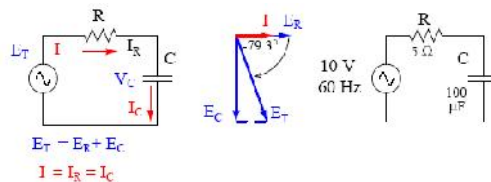

	R	C	Total	
E	$343.11m + j1.8203$ $1.8523 \angle 79.325^\circ$	$9.6509 - j1.8203$ $9.8269 \angle -10.675^\circ$	$10 + j0$ $10 \angle 0^\circ$	Volts
I	$68.623m + j364.06m$ $370.5m \angle 79.325^\circ$	$68.623m + j364.06m$ $370.5m \angle 79.325^\circ$	$68.623m + j364.06m$ $370.5m \angle 79.325^\circ$	Amps
Z	$5 + j0$ $5 \angle 0^\circ$	$0 - j26.5258$ $26.5258 \angle -90^\circ$	$5 - j26.5258$ $26.993 \angle -79.325^\circ$	Ohms

Ohm's Law
 $E = IZ$

Ohm's Law
 $E = IZ$

As it can be considered easily, the phase shift is 79.325 degrees in this circuit whereas in the circuit that has only one capacitor it was 90 degrees.


The current and the voltage on the resistor is on the same phase as it is mentioned.

However, the current on a capacitor leads voltage by 90 degrees.

Dr. Levent ÇETİN

L02 Alternating Voltage and Current

AC circuit –RC in parallel

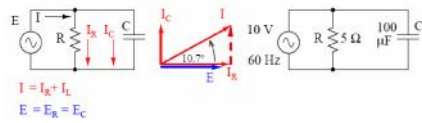

	R	C	Total	
E			$10 + j0$ $10 \angle 0^\circ$	Volts
I				Amps
Z	$5 + j0$ $5 \angle 0^\circ$	$0 - j26.5258$ $26.5258 \angle -90^\circ$		Ohms


	R	C	Total	
E	$10 + j0$ $10 \angle 0^\circ$	$10 + j0$ $10 \angle 0^\circ$	$10 + j0$ $10 \angle 0^\circ$	Volts
I				Amps
Z	$5 + j0$ $5 \angle 0^\circ$	$0 - j26.5258$ $26.5258 \angle -90^\circ$		Ohms

Rule of parallel circuits:
 $E_{total} = E_R = E_C$

Dr. Levent ÇETİN

L02 Alternating Voltage and Current

AC circuit –RC in parallel

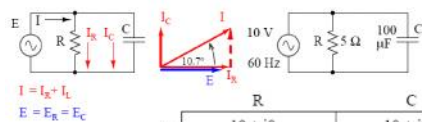

	R	C	Total	
E	$10 + j0$ $10 \angle 0^\circ$	$10 + j0$ $10 \angle 0^\circ$	$10 + j0$ $10 \angle 0^\circ$	Volts
I	$2 + j0$ $2 \angle 0^\circ$	$0 + j376.99m$ $376.99m \angle 90^\circ$		Amps
Z	$5 + j0$ $5 \angle 0^\circ$	$0 - j26.5258$ $26.5258 \angle -90^\circ$		Ohms

Ohm's Law
 $I = \frac{E}{Z}$

	R	C	Total	
E	$10 + j0$ $10 \angle 0^\circ$	$10 + j0$ $10 \angle 0^\circ$	$10 + j0$ $10 \angle 0^\circ$	Volts
I	$2 + j0$ $2 \angle 0^\circ$	$0 + j376.99m$ $376.99m \angle 90^\circ$	$2 + j376.99m$ $2.0352 \angle 10.675^\circ$	Amps
Z	$5 + j0$ $5 \angle 0^\circ$	$0 - j26.5258$ $26.5258 \angle -90^\circ$		Ohms

Rule of parallel circuits:
 $I_{total} = I_R + I_C$

Dr. Levent ÇETİN

L02 Alternating Voltage and Current

AC circuit –RC in parallel

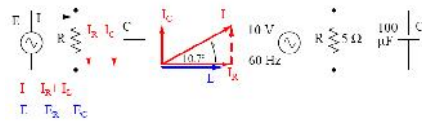


Figure 4.14: Parallel R-C circuit.

	R	C	Total	
E	$10 + j0$	$10 + j0$	$10 + j0$	Volts
	$10 \angle 0^\circ$	$10 \angle 0^\circ$	$10 \angle 0^\circ$	
I	$2 + j0$	$0 + j376.99\text{mA}$	$2 + j376.99\text{mA}$	Amps
	$2 \angle 0^\circ$	$376.99\text{mA} \angle 90^\circ$	$2.0552 \angle 10.675^\circ$	
Z	$5 + j0$	$0 - j26.5258$	$4.8284 - j910.14\text{m}$	Ohms
	$5 \angle 0^\circ$	$26.5258 \angle -90^\circ$	$4.9135 \angle -10.675^\circ$	

Ohm's Law or Rule of parallel circuits.

$$Z = \frac{E}{I} \quad \text{or} \quad Z_{\text{total}} = \frac{1}{\frac{1}{Z_R} + \frac{1}{Z_C}}$$

Dr. Levent ÇETİN

L02 Alternating Voltage and Current

AC circuit –RLC in series

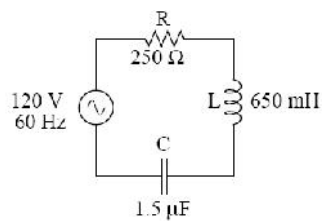


Figure 5.2: Example series R, L, and C circuit.

$$X_L = 2\pi fL$$

$$X_L = (2)(\pi)(60 \text{ Hz})(650 \text{ mH})$$

$$X_L = 245.04 \Omega$$

$$X_C = \frac{1}{2\pi fC}$$

$$X_C = \frac{1}{(2)(\pi)(60 \text{ Hz})(1.5 \mu\text{F})}$$



$$X_C = 1.7684 \text{ k}\Omega$$

$$Z_R = 250 + j0 \Omega \quad \text{or} \quad 250 \Omega \angle 0^\circ$$

$$Z_L = 0 + j245.04 \Omega \quad \text{or} \quad 245.04 \Omega \angle 90^\circ$$

$$Z_C = 0 - j1.7684 \text{ k}\Omega \quad \text{or} \quad 1.7684 \text{ k}\Omega \angle -90^\circ$$

Dr. Levent ÇETİN

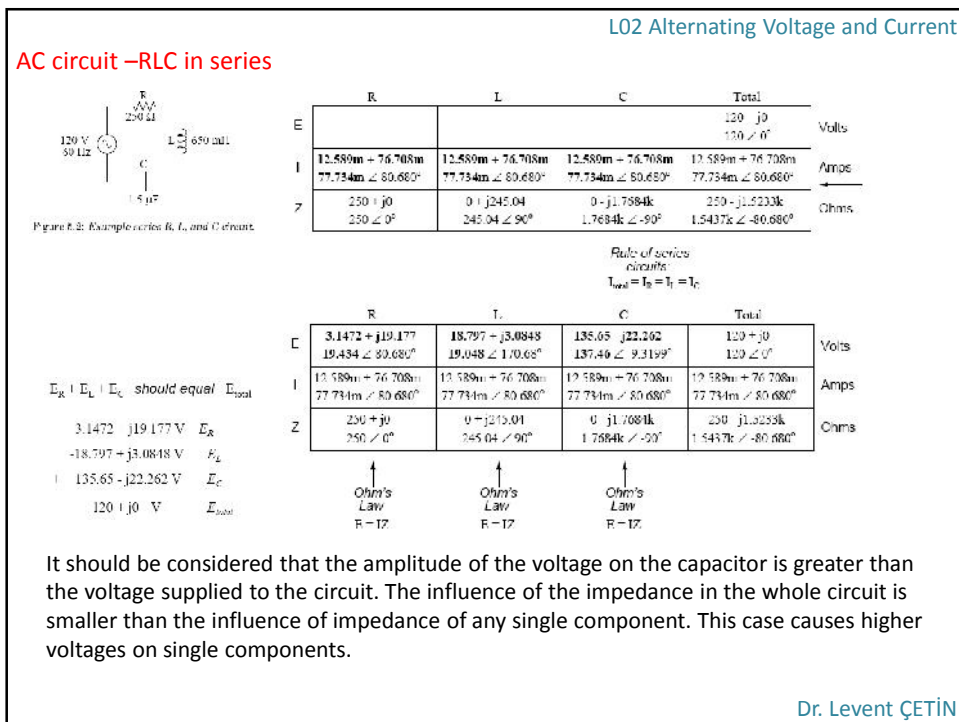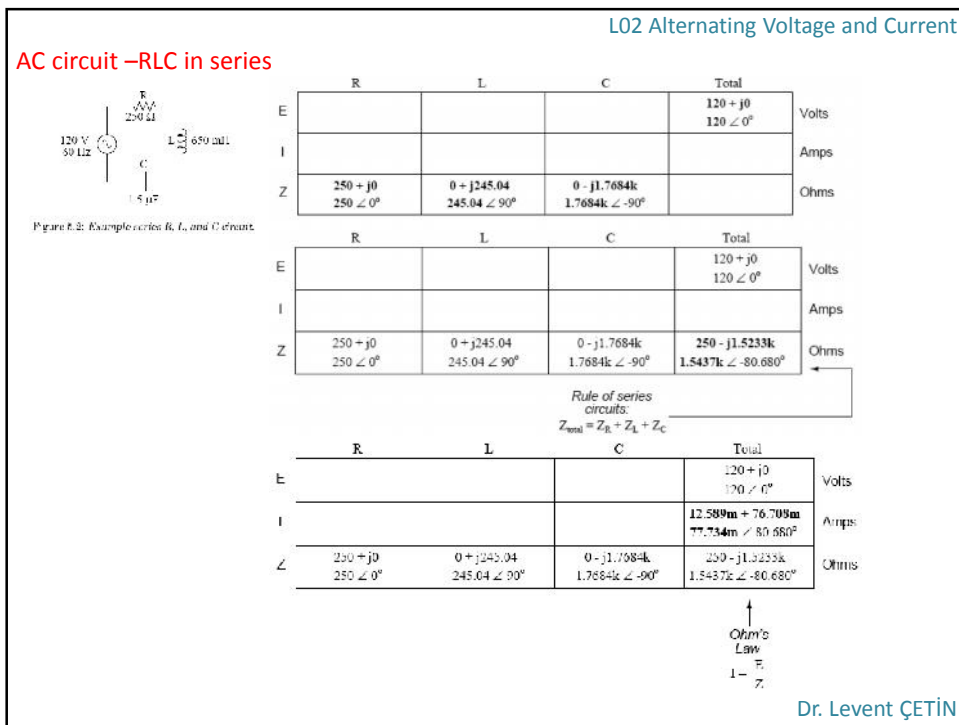

L02 Alternating Voltage and Current

AC circuit –RLC in parallel


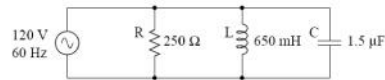


Figure 5.5: Example R, L, and C parallel circuit.

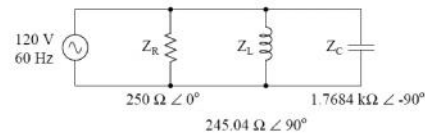

	R	L	C	Total	
E				$120 + j0$ $120 \angle 0^\circ$	Volts
I					Amps
Z	$250 + j0$ $250 \angle 0^\circ$	$0 + j245.04$ $245.04 \angle 90^\circ$	$0 - j1.7684k$ $1.7684k \angle -90^\circ$		Ohms

	R	L	C	Total	
E	$120 + j0$ $120 \angle 0^\circ$	$120 - j0$ $120 \angle 0^\circ$	$120 + j0$ $120 \angle 0^\circ$	$120 + j0$ $120 \angle 0^\circ$	Volts
I					Amps
Z	$250 + j0$ $250 \angle 0^\circ$	$0 - j245.04$ $245.04 \angle 90^\circ$	$0 - j1.7684k$ $1.7684k \angle -90^\circ$		Ohms

Rule of parallel circuits:
 $\frac{1}{Z_{total}} = \frac{1}{Z_R} + \frac{1}{Z_L} + \frac{1}{Z_C}$

Dr. Levent ÇETİN

L02 Alternating Voltage and Current

AC circuit –RLC in parallel

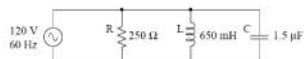


Figure 5.5: Example R, L, and C parallel circuit.

	R	L	C	Total	
E	$120 + j0$ $120 \angle 0^\circ$	$120 + j0$ $120 \angle 0^\circ$	$120 + j0$ $120 \angle 0^\circ$	$120 + j0$ $120 \angle 0^\circ$	Volts
I	$480m + j0$ $480m \angle 0^\circ$	$0 - j489.71m$ $489.71m \angle -90^\circ$	$0 + j67.858m$ $67.858m \angle 90^\circ$		Amps
Z	$250 + j0$ $250 \angle 0^\circ$	$0 + j245.04$ $245.04 \angle 90^\circ$	$0 - j1.7684k$ $1.7684k \angle -90^\circ$		Ohms

Ohm's Law
 $I = \frac{E}{Z}$

Ohm's Law
 $I = \frac{E}{Z}$


Ohm's Law
 $I = \frac{E}{Z}$

	R	L	C	Total	
E	$120 + j0$ $120 \angle 0^\circ$	$120 + j0$ $120 \angle 0^\circ$	$120 + j0$ $120 \angle 0^\circ$	$120 + j0$ $120 \angle 0^\circ$	Volts
I	$480m + j0$ $480 \angle 0^\circ$	$0 - j489.71m$ $489.71m \angle -90^\circ$	$0 + j67.858m$ $67.858m \angle 90^\circ$	$480m - j421.85m$ $639.03m \angle -41.31^\circ$	Amps
Z	$250 + j0$ $250 \angle 0^\circ$	$0 + j245.04$ $245.04 \angle 90^\circ$	$0 - j1.7684k$ $1.7684k \angle -90^\circ$	$141.05 - j123.96$ $187.79 \angle -41.31^\circ$	Ohms

Dr. Levent ÇETİN

L02 Alternating Voltage and Current

AC circuit –Complex Circuit

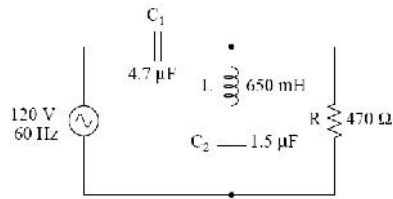

Reactances and Resistances:

$X_{C1} = \frac{1}{2\pi f C_1}$	$X_L = 2\pi f L$
$X_{C1} = \frac{1}{(2)(\pi)(60 \text{ Hz})(4.7 \mu\text{F})}$	$X_L = (2)(\pi)(60 \text{ Hz})(650 \text{ mH})$
$X_{C1} = 564.38 \Omega$	$X_L = 245.04 \Omega$
$X_{C2} = \frac{1}{2\pi f C_2}$	$R = 470 \Omega$
$X_{C2} = \frac{1}{(2)(\pi)(60 \text{ Hz})(1.5 \mu\text{F})}$	
$X_{C2} = 1.7684 \text{ k}\Omega$	

$$Z_{C1} = 0 - j564.38 \Omega \text{ or } 564.38 \Omega \angle -90^\circ$$

$$Z_L = 0 + j245.04 \Omega \text{ or } 245.04 \Omega \angle 90^\circ$$


$$Z_{C2} = 0 - j1.7684 \text{ k}\Omega \text{ or } 1.7684 \text{ k}\Omega \angle -90^\circ$$

$$Z_R = 470 + j0 \Omega \text{ or } 470 \Omega \angle 0^\circ$$

Dr. Levent ÇETİN

L02 Alternating Voltage and Current

AC circuit –Complex Circuit

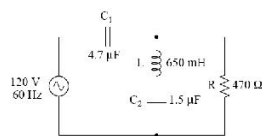

	C_1	L	C_2	R	Total	
E					$120 \angle 0^\circ$	Volts
I						Amps
Z	$0 - j564.38 \Omega$ $564.38 \angle -90^\circ$	$0 + j245.04 \Omega$ $245.04 \angle 90^\circ$	$0 - j1.7684 \text{ k}\Omega$ $1.7684 \angle -90^\circ$	$470 + j0 \Omega$ $470 \angle 0^\circ$		Ohms

The calculation of impedance in this circuit should be completed step by step.

First, serial connection branch of C_2 and L ,

afterwards the parallel branch of resistor and last the serial capacitor effects should be calculated.

	$L \leftrightarrow C_2$	$R \parallel (L \leftrightarrow C_2)$	Total $C_1 \leftrightarrow [R \parallel (L \leftrightarrow C_2)]$	
E			$120 \angle 0^\circ$	Volts
I				Amps
Z	$0 - j1.5233 \text{ k}\Omega$ $1.5233 \angle -90^\circ$	$429.15 - j132.41 \Omega$ $449.11 \angle -17.14^\circ$	$429.15 - j699.79 \Omega$ $818.34 \angle -58.571^\circ$	Ohms

↑
Rule of series circuits:
 $Z_{L \leftrightarrow C_2} = Z_L + Z_{C_2}$


↑
Rule of parallel circuits:
 $Z_{R \parallel (L \leftrightarrow C_2)} = \frac{1}{\frac{1}{Z_R} + \frac{1}{Z_{L \leftrightarrow C_2}}}$

↑
Rule of series circuits:
 $Z_{total} = Z_{C_1} + Z_{R \parallel (L \leftrightarrow C_2)}$

Dr. Levent ÇETİN

L02 Alternating Voltage and Current

AC circuit –Complex Circuit

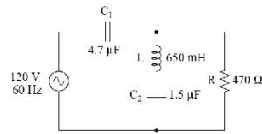Calculate current drawn from source and passing through C_1

	$L \leftrightarrow C_2$	$R // (L \leftrightarrow C_2)$	$C_1 \leftrightarrow [R // (L \leftrightarrow C_2)]$	
E			$120 + j0$ $120 \angle 0^\circ$	Volts
I			$76.899\text{mA} + j124.86\text{mA}$ $146.64\text{mA} \angle 58.371^\circ$	Amps
Z	$0 - j1.5233\text{k}$ $1.5233\text{k} \angle -90^\circ$	$429.15 - j132.41$ $449.11 \angle -17.147^\circ$	$429.15 - j696.79$ $818.34 \angle -58.371^\circ$	Ohms

Ohm's Law
 $I = \frac{E}{Z}$

Same current is passing through $L \leftrightarrow C_2$ branch


	$L \leftrightarrow C_2$	$R // (L \leftrightarrow C_2)$	$C_1 \leftrightarrow [R // (L \leftrightarrow C_2)]$	
E			$120 + j0$ $120 \angle 0^\circ$	Volts
I			$76.899\text{mA} + j124.86\text{mA}$ $146.64\text{mA} \angle 58.371^\circ$	Amps
Z	$0 - j1.5233\text{k}$ $1.5233\text{k} \angle -90^\circ$	$429.15 - j132.41$ $449.11 \angle -17.147^\circ$	$429.15 - j696.79$ $818.34 \angle -58.371^\circ$	Ohms

Rule of series circuits:
 $I_{\text{total}} = I_{C1} = I_{R \leftrightarrow (L \leftrightarrow C2)}$

Dr. Levent ÇETİN

L02 Alternating Voltage and Current

AC circuit –Complex Circuit

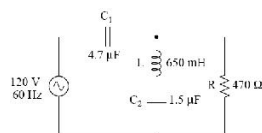Voltage drop on $L \leftrightarrow C_2$ branch

	$L \leftrightarrow C_2$	$R // (L \leftrightarrow C_2)$	$C_1 \leftrightarrow [R // (L \leftrightarrow C_2)]$	
E			$120 + j0$ $120 \angle 0^\circ$	Volts
I			$76.899\text{mA} + j124.86\text{mA}$ $146.64\text{mA} \angle 58.371^\circ$	Amps
Z	$0 - j1.5233\text{k}$ $1.5233\text{k} \angle -90^\circ$	$429.15 - j132.41$ $449.11 \angle -17.147^\circ$	$429.15 - j696.79$ $818.34 \angle -58.371^\circ$	Ohms

Ohm's Law
 $E = IZ$

Same Voltage drops on parallel R branch


	$L \leftrightarrow C_2$	$R // (L \leftrightarrow C_2)$	$C_1 \leftrightarrow [R // (L \leftrightarrow C_2)]$	
E	$49.533 - j43.400$ $65.857 \angle 41.225^\circ$	$49.533 + j43.400$ $65.857 \angle 41.225^\circ$	$120 + j0$ $120 \angle 0^\circ$	Volts
I			$76.899\text{mA} + j124.86\text{mA}$ $146.64\text{mA} \angle 58.371^\circ$	Amps
Z	$0 - j1.5233\text{k}$ $1.5233\text{k} \angle -90^\circ$	$429.15 - j132.41$ $449.11 \angle -17.147^\circ$	$429.15 - j696.79$ $818.34 \angle -58.371^\circ$	Ohms

Rule of parallel circuits:
 $E_{R // (L \leftrightarrow C2)} = E_R = E_{L \leftrightarrow C2}$

Dr. Levent ÇETİN

L02 Alternating Voltage and Current

AC circuit –Complex Circuit

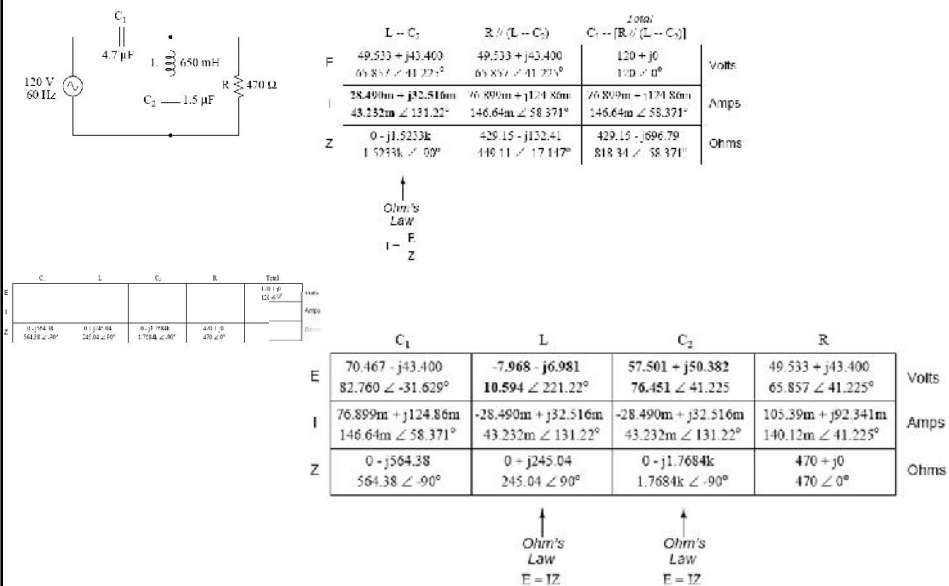

Dr. Levent ÇETİN


L02 Alternating Voltage and Current

Power in AC circuit

Since it was mentioned, there is a phase shift between current and voltage in AC circuits. The reason is the complex number impedance as it was stated. So there are three definitions in AC circuits which are related with power. These are:

- True power (active power),
- Reactive power,
- Apparent power.

Impedance Calculations:

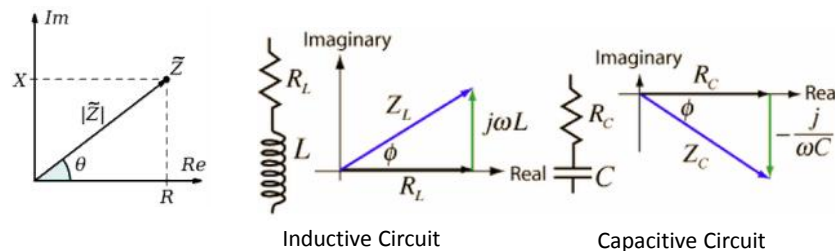

Dr. Levent ÇETİN

L02 Alternating Voltage and Current

Power in AC circuit

$$P = \text{true power} \quad P = I^2 R \quad P = \frac{E^2}{R}$$


Measured in units of **Watts**

$$Q = \text{reactive power} \quad Q = I^2 X \quad Q = \frac{E^2}{X}$$

Measured in units of **Volt-Amps-Reactive (VAR)**

$$S = \text{apparent power} \quad S = I^2 Z \quad S = \frac{E^2}{Z} \quad S = IE$$


Measured in units of **Volt-Amps (VA)**

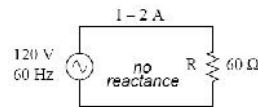

$$P = \text{true power} = I^2 R = 240 \text{ W}$$

$$Q = \text{reactive power} = I^2 X = 0 \text{ VAR}$$
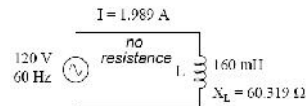
$$S = \text{apparent power} = I^2 Z = 240 \text{ VA}$$



$$P = \text{true power} = I^2 R = 0 \text{ W}$$

$$Q = \text{reactive power} = I^2 X = 238.73 \text{ VAR}$$

$$S = \text{apparent power} = I^2 Z = 238.73 \text{ VA}$$

Dr. Levent ÇETİN

L02 Alternating Voltage and Current

Power in AC circuit

$$P = \text{true power} \quad P = I^2 R \quad P = \frac{E^2}{R}$$

Measured in units of **Watts**

$$Q = \text{reactive power} \quad Q = I^2 X \quad Q = \frac{E^2}{X}$$


Measured in units of **Volt-Amps-Reactive (VAR)**

$$S = \text{apparent power} \quad S = I^2 Z \quad S = \frac{E^2}{Z} \quad S = IE$$

Measured in units of **Volt-Amps (VA)**

The power quantities are scalar quantities. if we consider the 90 degrees of direction angle between the resistor and the reactance and phase shift in the circuit.

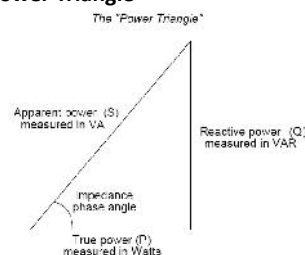This perpendicular triangle is called as 'Power Triangle'



A part of the power cannot be converted to electrical work in an AC circuit.

The generated effective power is just as the true power.

Power factor is the cosine of the angle between the true and apparent powers ($\cos \phi$).

This value is equal to 1 in only circuits those have just resistors. But if there is a reactance, then the value is between 0 and 1.

Dr. Levent ÇETİN

L02 Alternating Voltage and Current

Power in AC circuit

$$P = \text{true power} \quad P = I^2 R \quad P = \frac{E^2}{R}$$


Measured in units of Watts

$$Q = \text{reactive power} \quad Q = I^2 X \quad Q = \frac{E^2}{X}$$

Measured in units of Volt-Amps-Reactance (VAR)

$$S = \text{apparent power} \quad S = I^2 Z \quad S = \frac{E^2}{Z} \quad S = IE$$

Measured in units of Volt-Amps (VA)

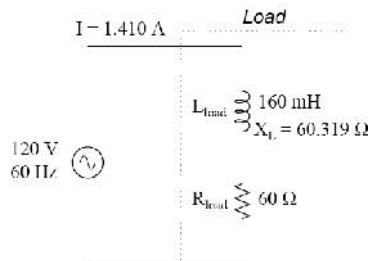

$$\text{Power factor} = \frac{\text{True power}}{\text{Apparent power}}$$

$$\text{Power factor} = \frac{119.365 \text{ W}}{169.256 \text{ VA}}$$

$$\text{Power factor} = 0.705$$

$$P = \text{true power} = I^2 R = 119.365 \text{ W}$$

$$Q = \text{reactive power} = I^2 X = 119.998 \text{ VAR}$$

$$S = \text{apparent power} = I^2 Z = 169.256 \text{ VA}$$

The power factor value shows that the **70.5 % of the power used from the grid is served for the purpose.**

Dr. Levent ÇETİN

L02 Alternating Voltage and Current

Compensation in AC circuit

$$P = \text{true power} \quad P = I^2 R \quad P = \frac{E^2}{R}$$


Measured in units of Watts

$$Q = \text{reactive power} \quad Q = I^2 X \quad Q = \frac{E^2}{X}$$

Measured in units of Volt-Amps-Reactance (VAR)

$$S = \text{apparent power} \quad S = I^2 Z \quad S = \frac{E^2}{Z} \quad S = IE$$

Measured in units of Volt-Amps (VA)

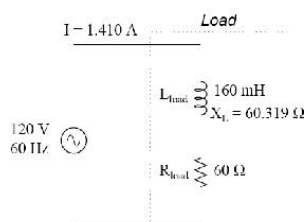

$$P = \text{true power} = I^2 R = 119.365 \text{ W}$$

$$Q = \text{reactive power} = I^2 X = 119.998 \text{ VAR}$$

$$S = \text{apparent power} = I^2 Z = 169.256 \text{ VA}$$

$$\text{Power factor} = \frac{\text{True power}}{\text{Apparent power}}$$

$$\text{Power factor} = \frac{119.365 \text{ W}}{169.256 \text{ VA}}$$

$$\text{Power factor} = 0.705$$

The power factor value shows that the **70.5 % of the power used from the grid is served for the purpose.**

This situation is not wanted.

So, in circuit design stage, it must be noted that the power factor is approximately equal to 1.

For this reason, the capacitive and inductive reactance values should be approximately equal to each other.

If this is not possible, a capacitor or an inductor should be externally added to the circuit. **This improvement is called as compensation.**

Dr. Levent ÇETİN

L02 Alternating Voltage and Current

Compensation in AC circuit

$$P = \text{true power} \quad P = I^2 R \quad P = \frac{E^2}{R}$$


Measured in units of **Watts**

$$Q = \text{reactive power} \quad Q = I^2 X \quad Q = \frac{E^2}{X}$$

Measured in units of **Volt-Amps-Reactance (VAR)**

$$S = \text{apparent power} \quad S = I^2 Z \quad S = \frac{E^2}{Z} \quad S = IE$$

Measured in units of **Volt-Amps (VA)**

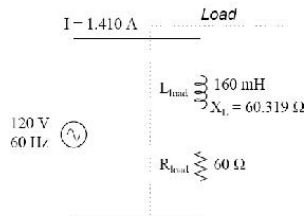

$$P = \text{true power} = I^2 R = 119.365 \text{ W}$$

$$Q = \text{reactive power} = I^2 X = 119.998 \text{ VAR}$$

$$S = \text{apparent power} = I^2 Z = 169.256 \text{ VA}$$

$$\text{Power factor} = \frac{\text{True power}}{\text{Apparent power}}$$

$$\text{Power factor} = \frac{119.365 \text{ W}}{169.256 \text{ VA}}$$

$$\text{Power factor} = 0.705$$

The circuit is inductive so a **parallel** capacitor should be added so that the total reactance of the circuit becomes approximately zero

$$Q = \frac{E^2}{X}$$

... solving for X ...

$$X = \frac{E^2}{Q}$$

$$X = \frac{(120 \text{ V})^2}{119.998 \text{ VAR}}$$

$$X = 120.002 \Omega$$

In parallel branches voltage is constant so the necessary reactance value can be calculated using voltage based power formula

Dr. Levent ÇETİN

L02 Alternating Voltage and Current

Compensation in AC circuit

$$P = \text{true power} \quad P = I^2 R \quad P = \frac{E^2}{R}$$


Measured in units of **Watts**

$$Q = \text{reactive power} \quad Q = I^2 X \quad Q = \frac{E^2}{X}$$

Measured in units of **Volt-Amps-Reactance (VAR)**

$$S = \text{apparent power} \quad S = I^2 Z \quad S = \frac{E^2}{Z} \quad S = IE$$

Measured in units of **Volt-Amps (VA)**

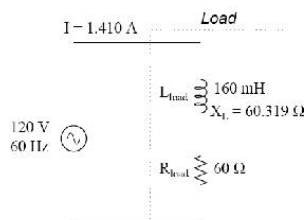

$$P = \text{true power} = I^2 R = 119.365 \text{ W}$$

$$Q = \text{reactive power} = I^2 X = 119.998 \text{ VAR}$$

$$S = \text{apparent power} = I^2 Z = 169.256 \text{ VA}$$

$$\text{Power factor} = \frac{\text{True power}}{\text{Apparent power}}$$

$$\text{Power factor} = \frac{119.365 \text{ W}}{169.256 \text{ VA}}$$

$$\text{Power factor} = 0.705$$

The calculated reactance value is used to find capacitor value

$$X_C = \frac{1}{2\pi fC}$$

... solving for C ...

$$C = \frac{1}{2\pi fX_C}$$

$$C = \frac{1}{2\pi(60 \text{ Hz})(120.002 \Omega)}$$

$$C = 22.105 \mu\text{F}$$

Dr. Levent ÇETİN

L02 Alternating Voltage and Current

Compensation in AC circuit

$$P = \text{true power} \quad P = I^2 R \quad P = \frac{E^2}{R}$$


Measured in units of Watts

$$Q = \text{reactive power} \quad Q = I^2 X \quad Q = \frac{E^2}{X}$$

Measured in units of Volt-Amps-Reactives (VAR)

$$S = \text{apparent power} \quad S = I^2 Z \quad S = \frac{E^2}{Z} \quad S = IE$$

Measured in units of Volt-Amps (VA)

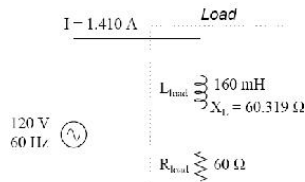

$$P = \text{true power} = I^2 R = 119.365 \text{ W}$$

$$Q = \text{reactive power} = I^2 X = 119.998 \text{ VAR}$$


$$S = \text{apparent power} = I^2 Z = 169.256 \text{ VA}$$

$$\text{Power factor} = \frac{\text{True power}}{\text{Apparent power}}$$

$$\text{Power factor} = \frac{119.365 \text{ W}}{169.256 \text{ VA}}$$

$$\text{Power factor} = 0.705$$

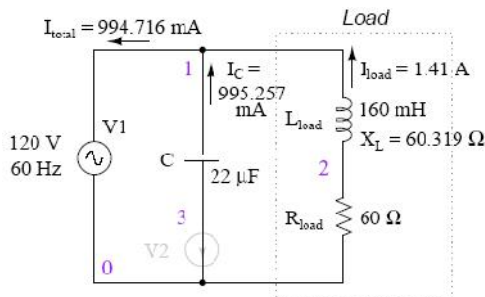The capacitor value found is not a standard value for capacitors, so the closest standard value should be chosen (22 μF) and connected in parallel with the circuit.



Dr. Levent ÇETİN

L02 Alternating Voltage and Current

Compensation in AC circuit

$$P = \text{true power} \quad P = I^2 R \quad P = \frac{E^2}{R}$$


Measured in units of Watts

$$Q = \text{reactive power} \quad Q = I^2 X \quad Q = \frac{E^2}{X}$$

Measured in units of Volt-Amps-Reactives (VAR)

$$S = \text{apparent power} \quad S = I^2 Z \quad S = \frac{E^2}{Z} \quad S = IE$$

Measured in units of Volt-Amps (VA)

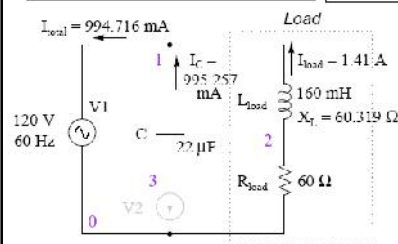

$$Z_{\text{total}} = Z_C // (Z_L + Z_R)$$

$$Z_{\text{total}} = (120.57 \angle -90^\circ) // (60.319 \angle 90^\circ + 60 \angle 0^\circ)$$

$$Z_{\text{total}} = 120.64 - j573.58 \text{ m}\Omega \quad \text{or} \quad 120.64 \angle 0.2724^\circ$$

$$P = \text{true power} = I^2 R = 119.365 \text{ W}$$

$$S = \text{apparent power} = I^2 Z = 119.366 \text{ VA}$$

$$\text{Power factor} = \frac{\text{True power}}{\text{Apparent power}}$$

$$\text{Power factor} = \frac{119.365 \text{ W}}{119.366 \text{ VA}}$$

$$\text{Power factor} = 0.9999887$$

this improvement made the power factor closer to 1. Besides, the current is decreased.

Dr. Levent ÇETİN